



ELENCO COMPONENTI

Vcc	12 V	R1	1	M Ω	trimmer
C1	22 μ F 25 V	R2	68	k Ω	1/4 W
C2	1000 μ F 25 V	R3	15	k Ω	1/4 W
C3	10 μ F 25 V	R4	5.6	k Ω	1/4 W
TR	BC 107	R5	1.5	k Ω	1/4 W
		R6	10	k Ω	potenziometro lineare

guadagno di tensione

$$A = 20 \lg \left(\frac{V_{out}}{V_{in}} \right) \text{ (dB)}$$