
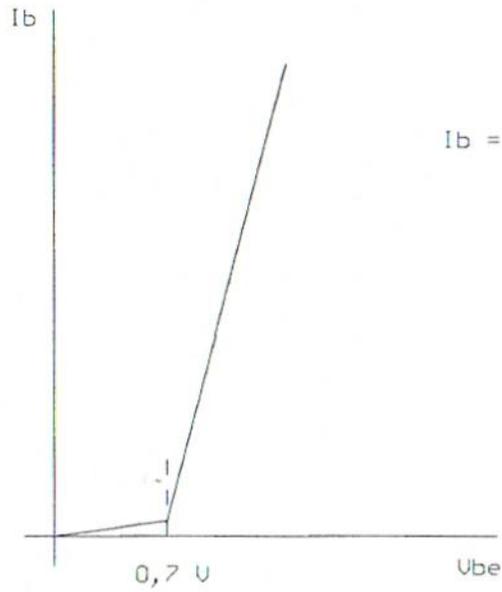


caratteristica d'ingresso

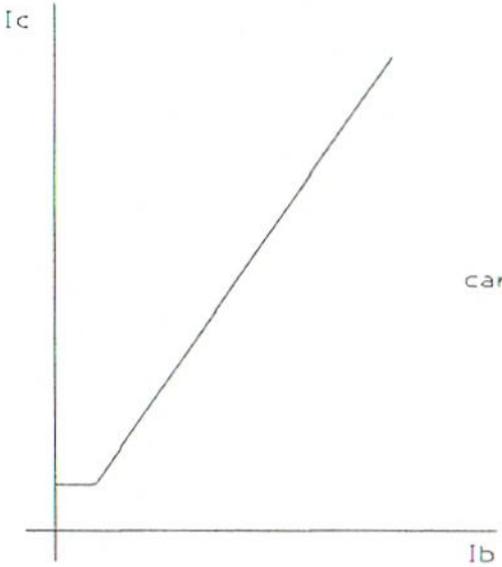


$$I_b = \frac{U_b - 0,7}{R_b}$$




caratteistica mutua

caratteristiche d'uscita

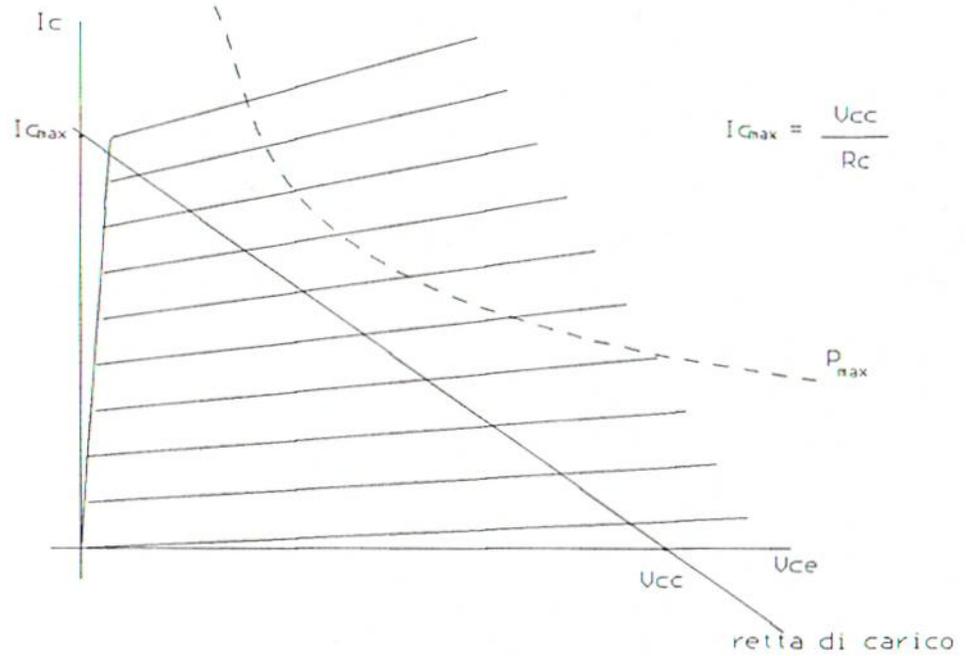


$$I_{Cmax} = \frac{U_{CC}}{R_c}$$

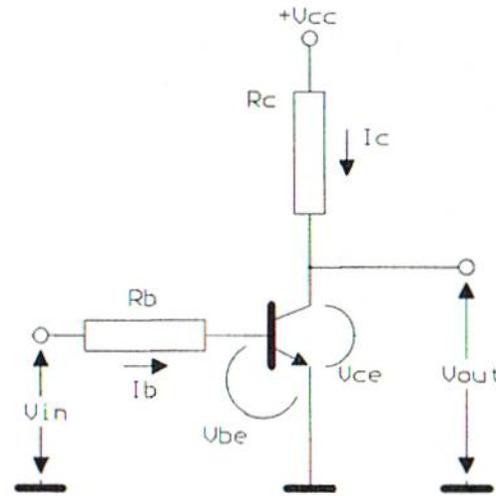

caratteristica mutua


caratteristiche d'uscita

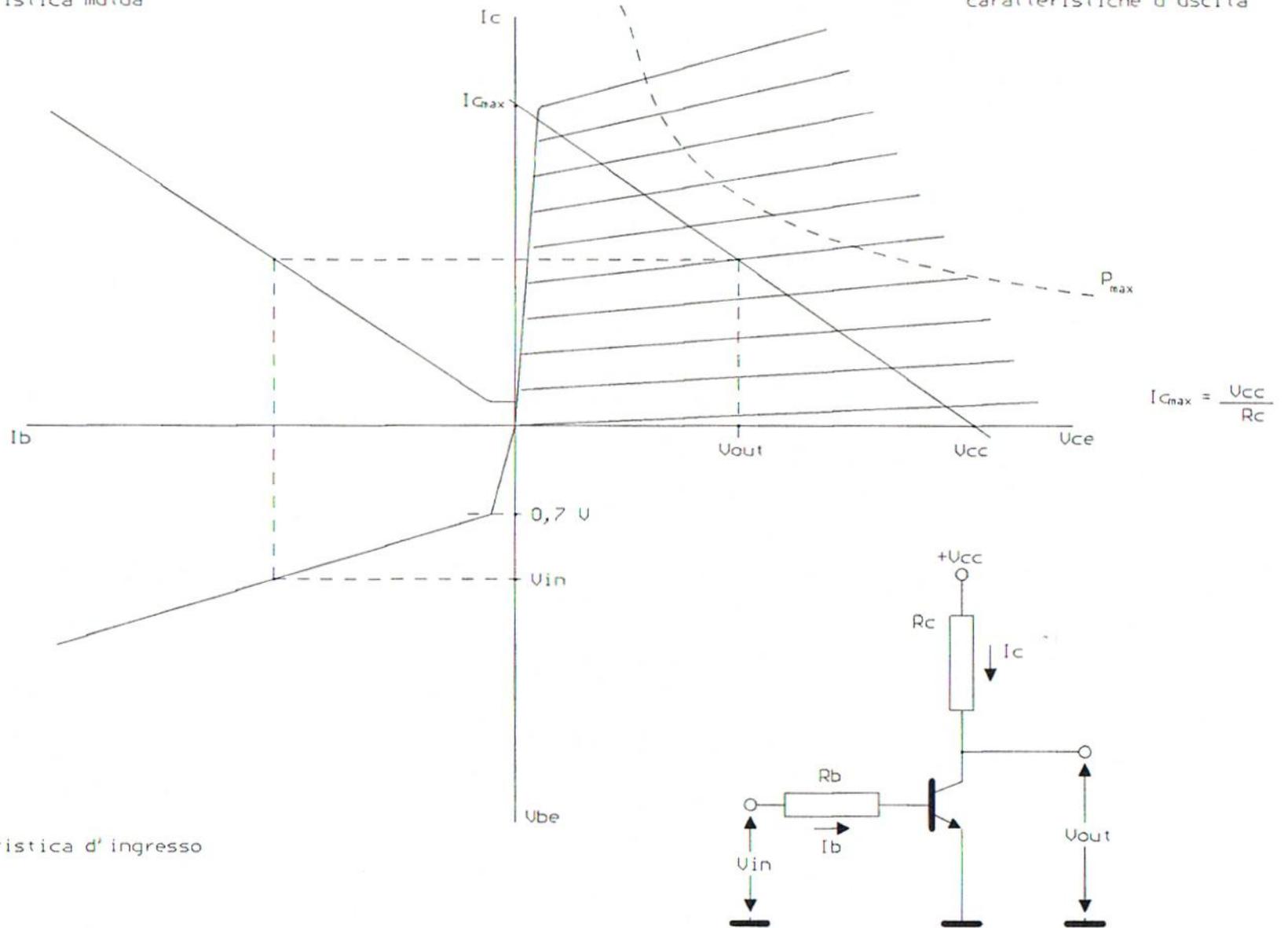

caratteristica d'ingresso

caratteristica mutua

caratteristiche d'uscita

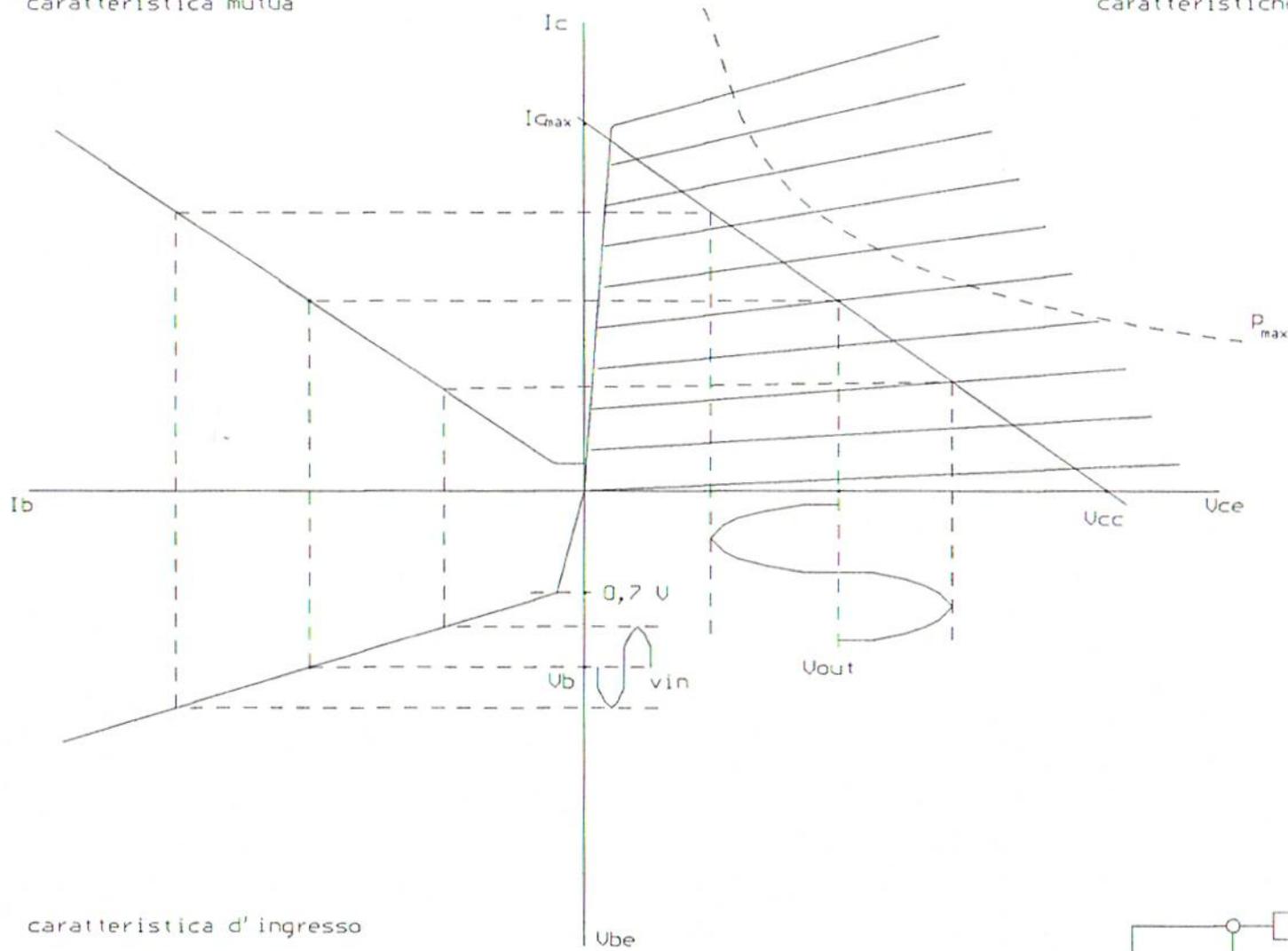

$$I_{Cmax} = \frac{U_{cc}}{R_c}$$

caratteristica d'ingresso

